

# Homework


- Reading
  - Tokheim, Chapter 3, 4, and 6.1 - 6.3
  - Logisim Website
- Machine Projects
  - Continue on mp3
- Labs
  - Continue in labs with your assigned section

# Combining Basic Logic Gates

- Decoders
- Encoders
- Selectors - Multiplexers
- ALUs
- Control Units
- Buses
- Simple computers

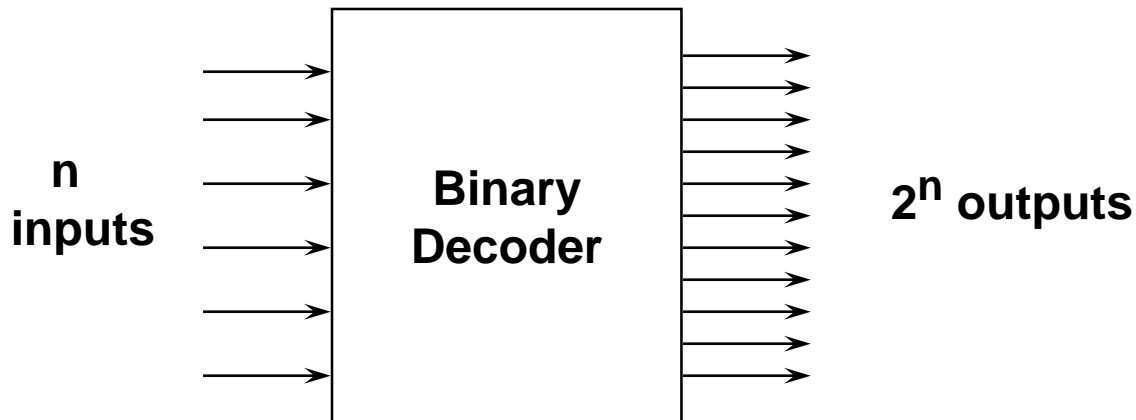
# Binary Decoder

- Logic with  $n$  input lines and  $2^n$  output lines
- Only one output is a 1 for any given input




# Building a Binary Decoder

- Start with a 2-bit decoder:

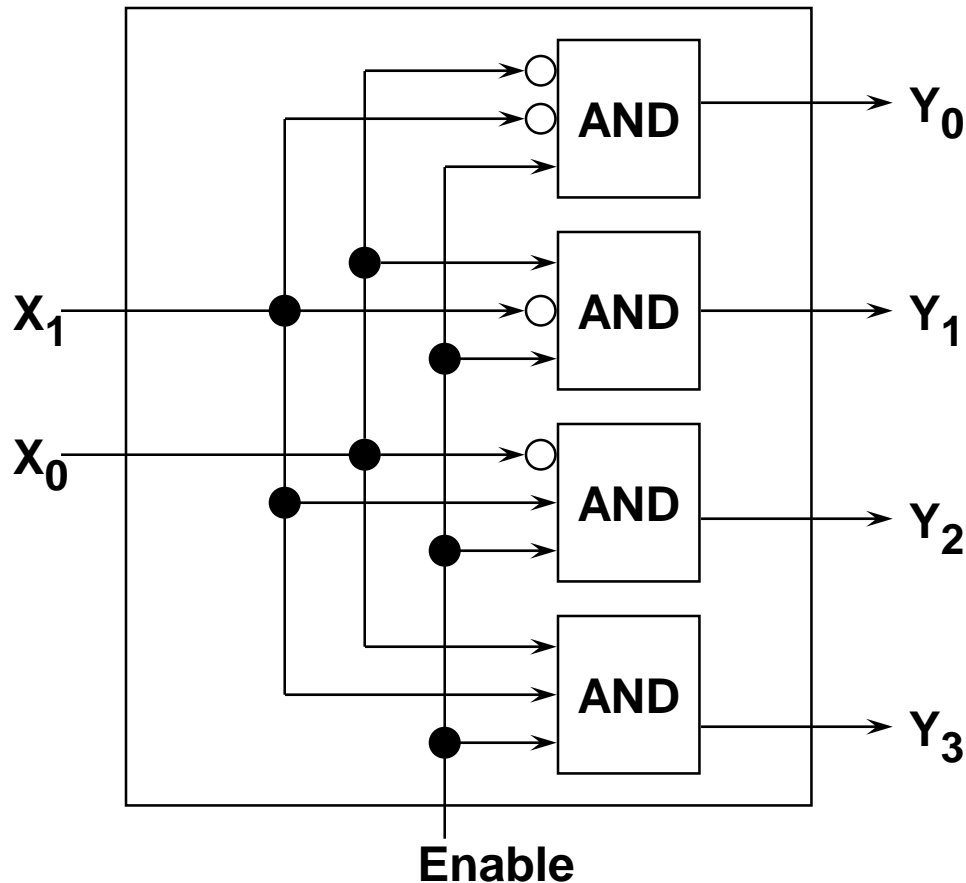


# Then Add Two to Make Three...

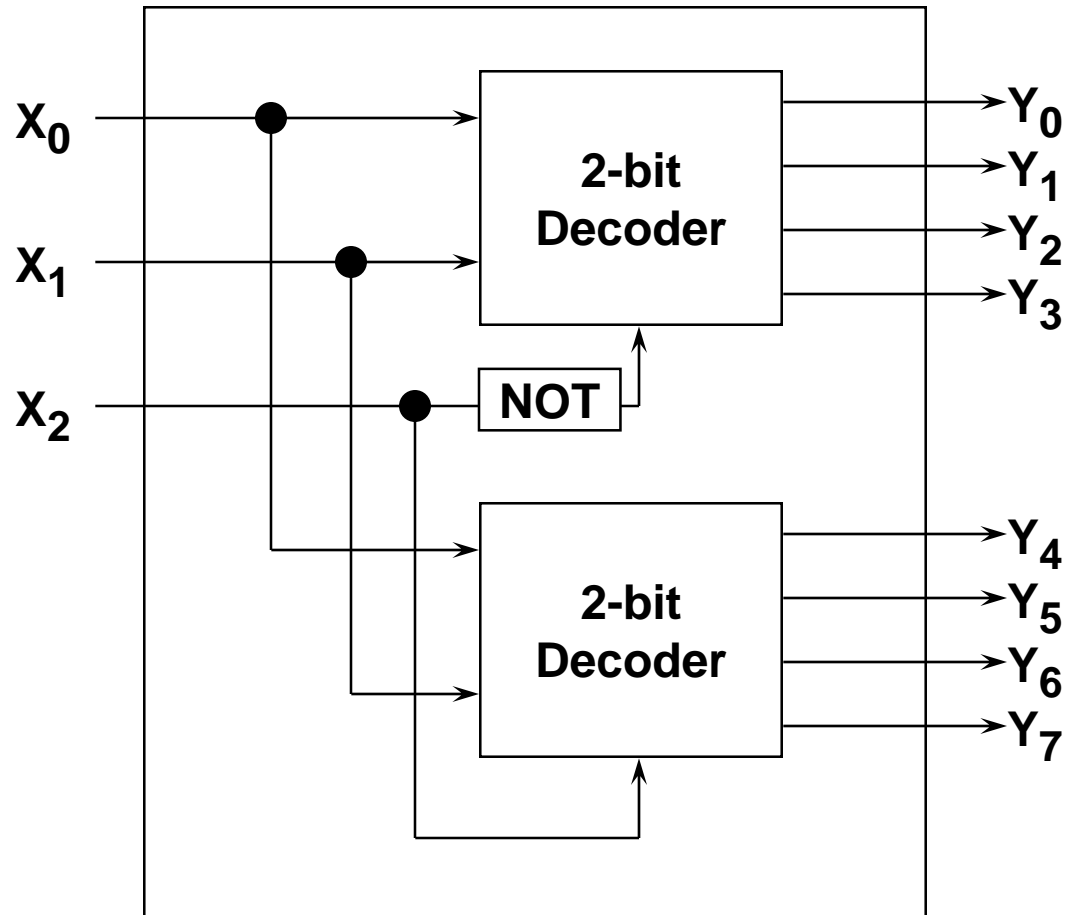

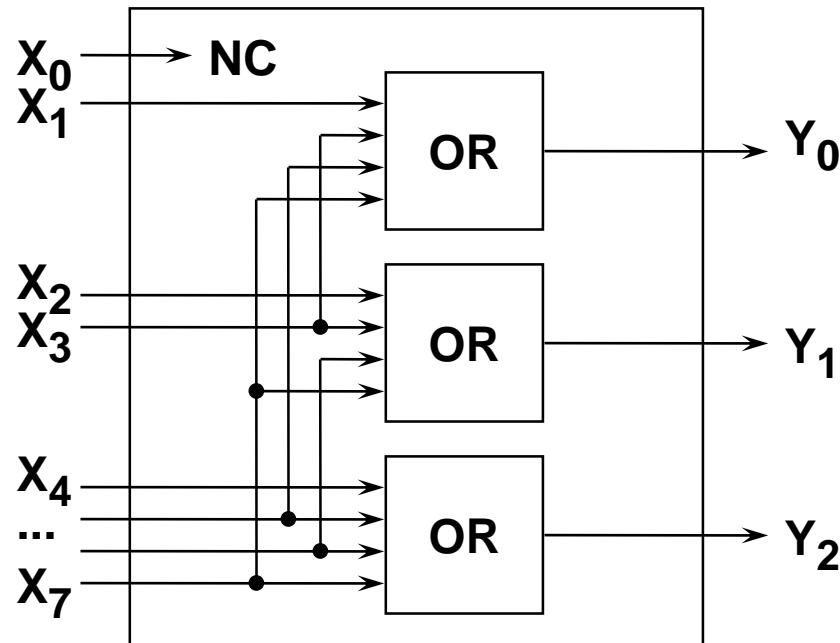
# Developing an Encoder

- If we can decode, then we need to encode
- Encode from 1 out of n into a binary weighted form
- A keyboard encoder does this



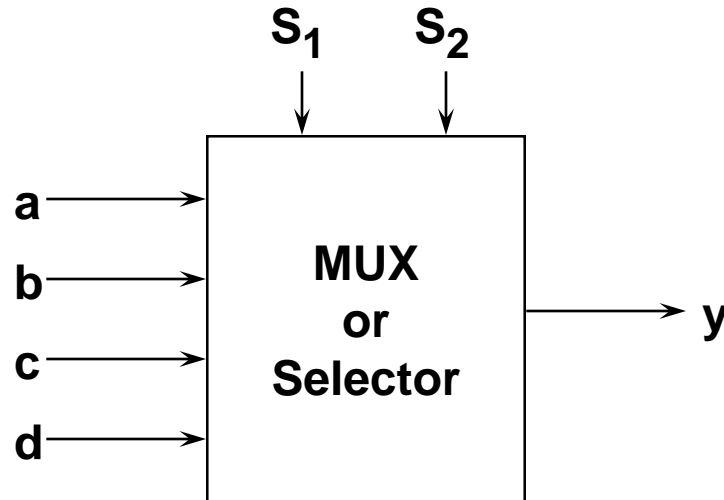
# Next Comes a Selector

- Like a switch; also called a multiplexer or MUX






- Again, build it up from simple basic logic gates

# A 1-bit Selector

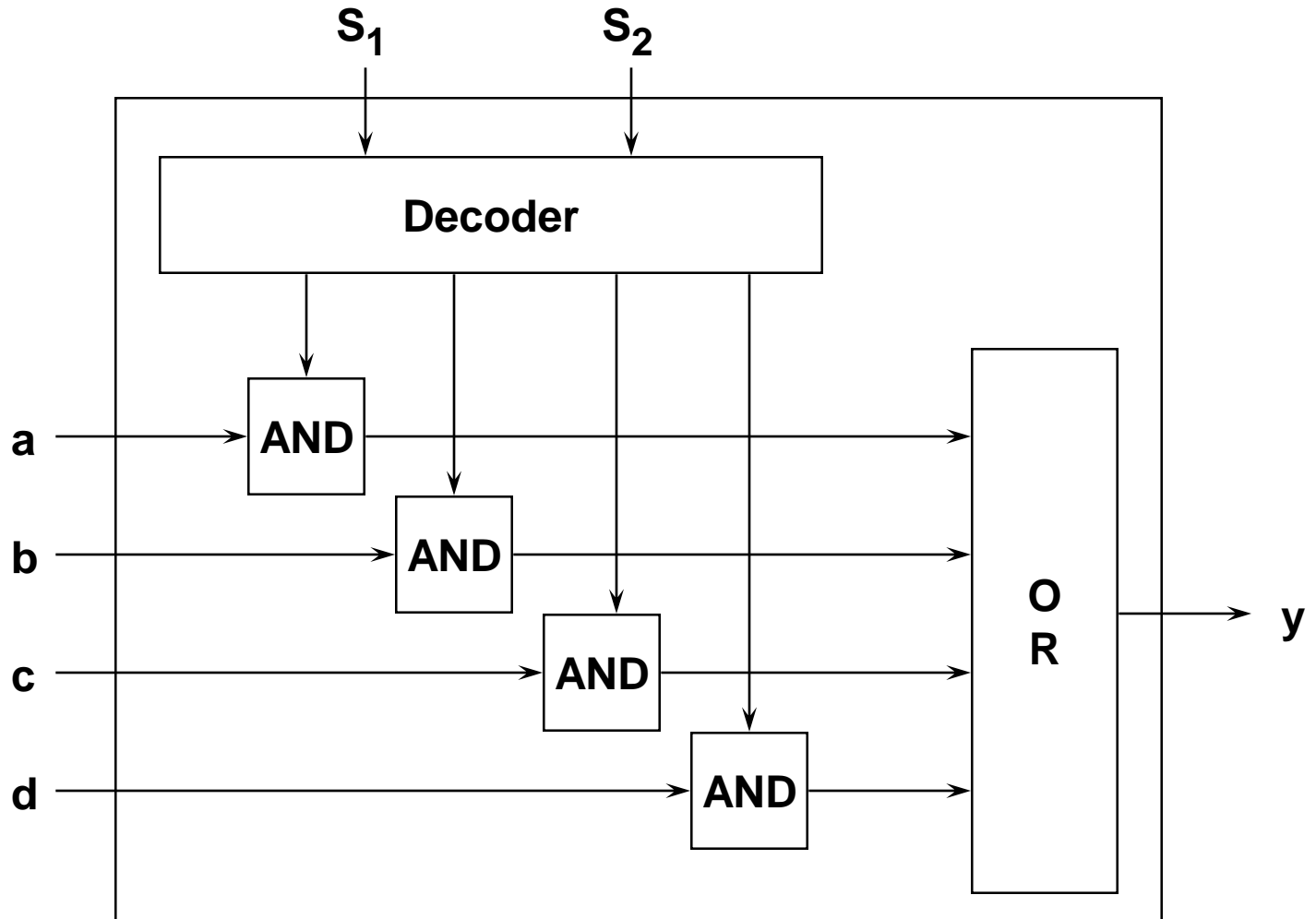




# A 4-bit Selector

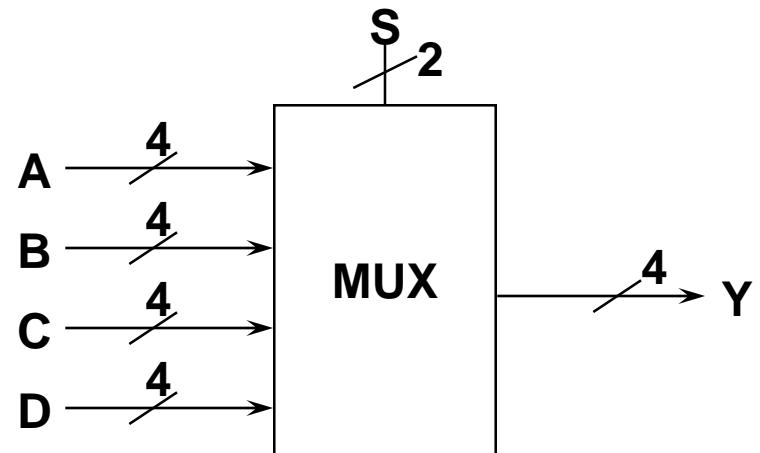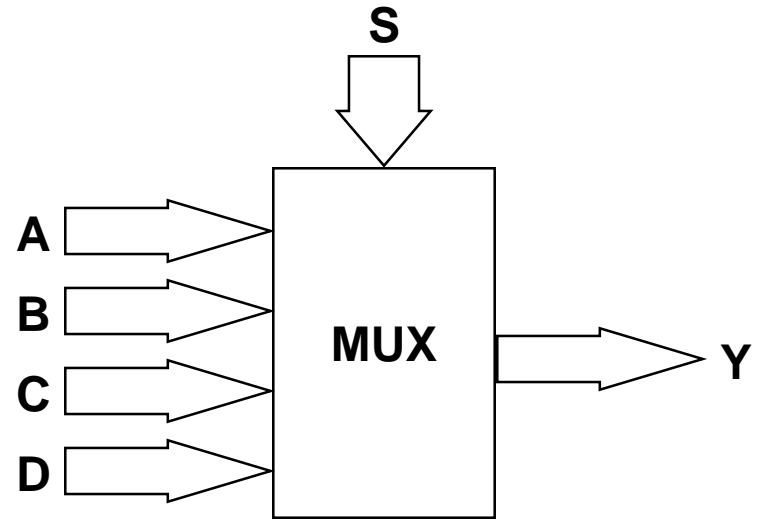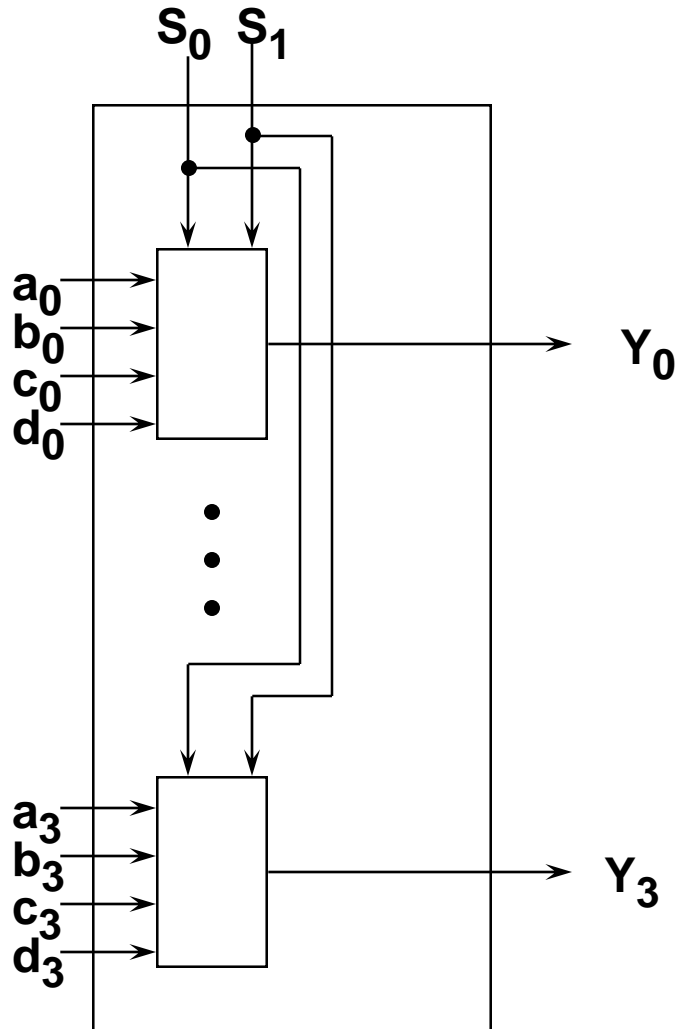
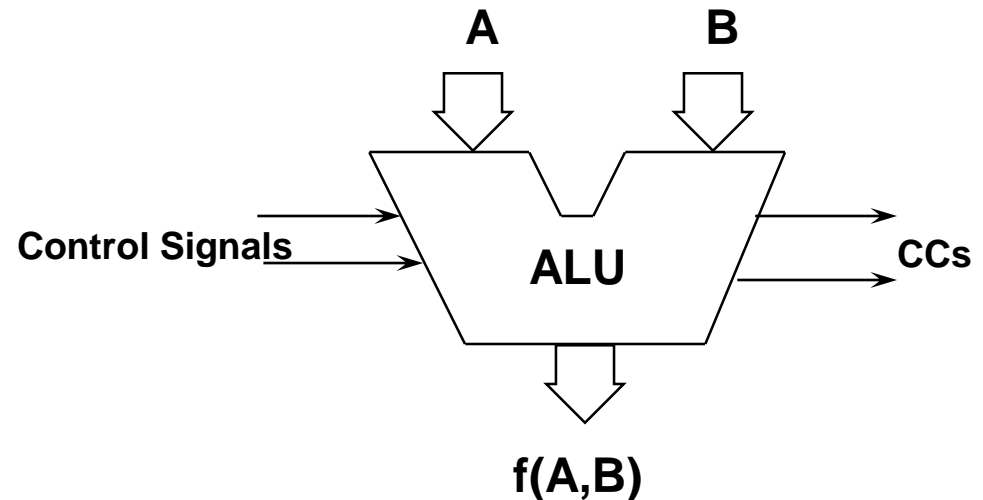
# The ALU Is Next

- Logical and arithmetic operations
- Variations in
  - Base
    - Binary
    - Decimal
    - BCD
  - Implementation
    - Serial
    - Parallel
    - Pipelined




# Simple Example - Binary Adder

- Develop a half-adder (HA)
- Use two HA's to build a full-adder (FA)

# The Half-Adder


$$\text{Sum} = (\bar{a} \bullet b) + (a \bullet \bar{b}) = (\bar{a} + \bar{b}) \bullet (a + b)$$

$$\text{Carry} = a \bullet b$$

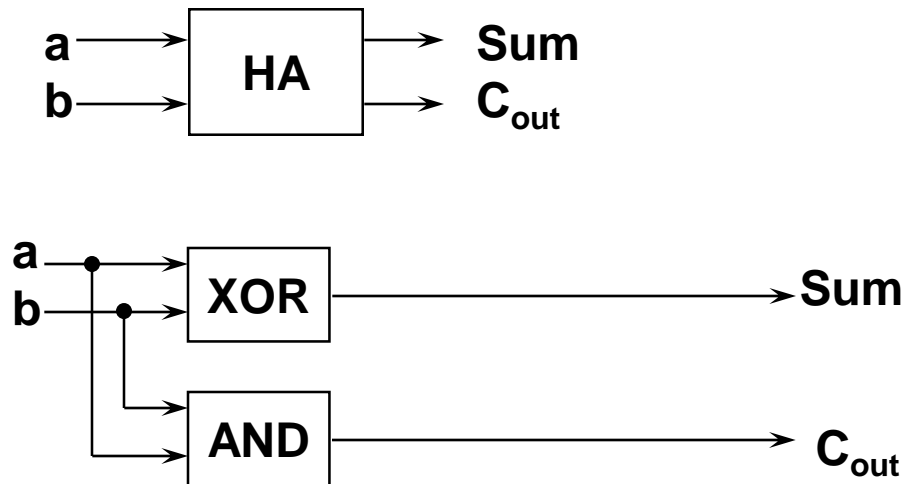


a	b	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


# From HA to FA

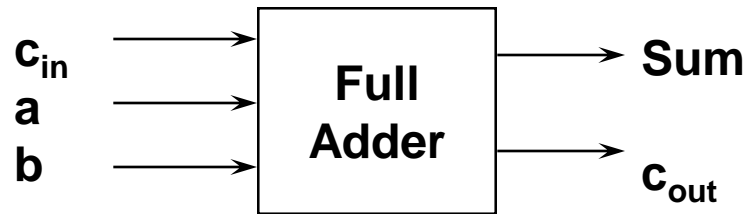

a	b	$c_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

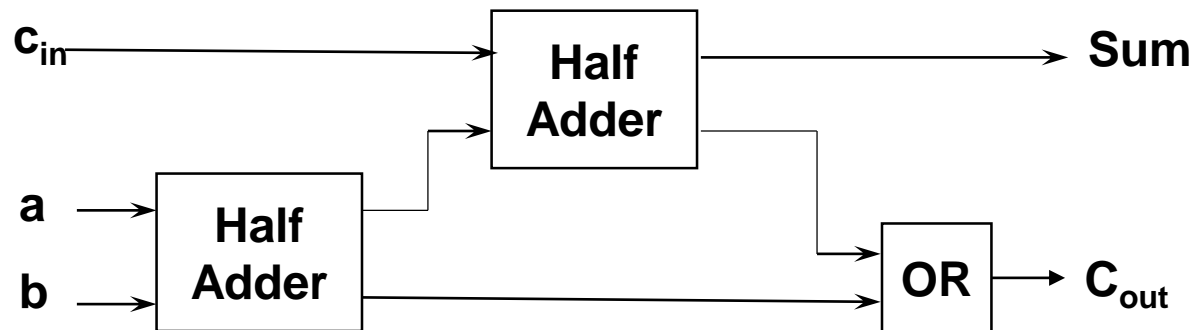

# Using Full Adders for Addition

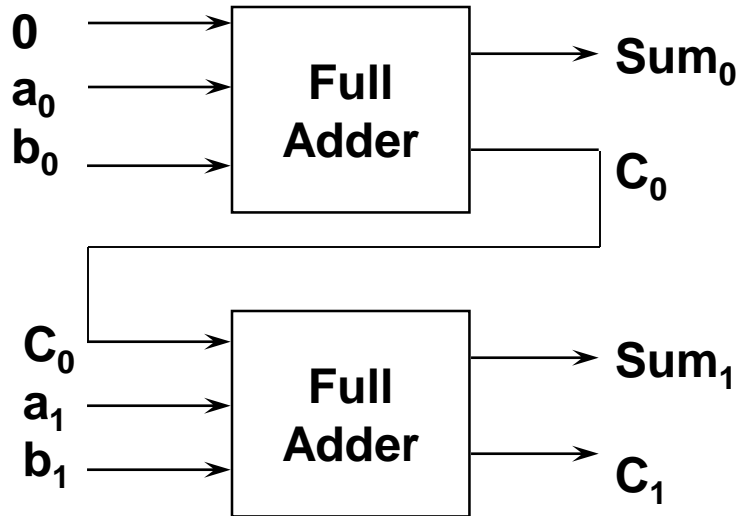


$$\begin{array}{r}
 00 \quad 00 \\
 + 11 \quad + 01 \\
 \hline
 (0)11 \quad (0)01
 \end{array}
 \qquad
 \begin{array}{r}
 11 \quad 11 \\
 + 01 \quad + 11 \\
 \hline
 (1)00 \quad (1)10
 \end{array}$$

a	b	$C_{in}$	$Sum_0$	$C_0$
<b>LSB</b>				
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
<b>MSBs</b>				
		$C_{n-1}$	$Sum_n$	$C_n$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Note: The carry flag value after the addition represents the N+1 bit value in the result
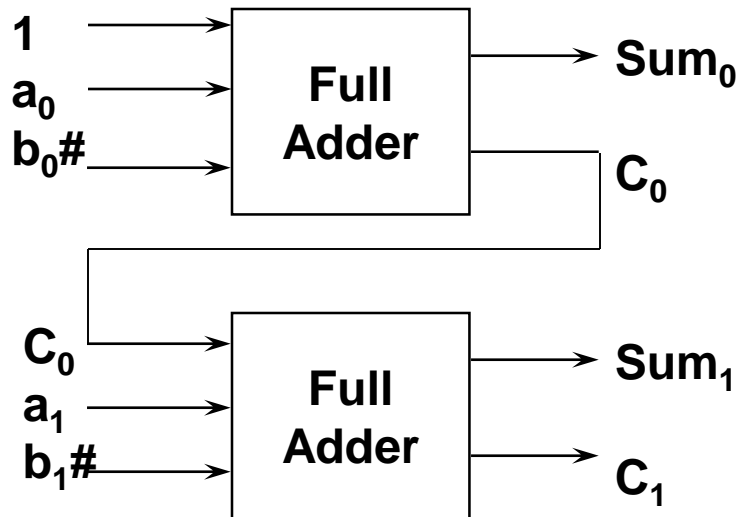
# Using Full Adders for Subtraction

$$\begin{aligned}
 \text{Difference} &= a - b \\
 &= a + (-b) \\
 &= a + (\sim b + 1) \\
 &= a + \sim b + 1
 \end{aligned}$$



$$\begin{array}{r}
 (1) 00 \quad 00 \\
 - 11 \quad + 01 \\
 \hline
 01 \quad (0) 01
 \end{array}
 \qquad
 \begin{array}{r}
 (0) 11 \quad 11 \\
 - 01 \quad + 11 \\
 \hline
 10 \quad (1) 10
 \end{array}$$

a	b#	$C_0$	Sum	$C_1$
<b>LSB</b>				
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1
<b>MSBs</b>				
		$C_{n-1}$		$C_n$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Note: The carry flag value after the  $\sim$  and addition is the opposite of the subtract borrow condition

# Configurable Add/Subtract ALU

